


PART 2**Program:**

```


module part2 (SW, KEY, LEDR);
    input [1:0] SW;
    input [0:0] KEY;
    output [9:0] LEDR;
    wire Clock, Resetn, w, z;
    reg [3:0] y_Q, Y_D;
    assign Clock = KEY[0];
    assign Resetn = SW[0];
    assign w = SW[1];
    parameter A = 4'b0000, B = 4'b0001, C = 4'b0010, D = 4'b0011, E = 4'b0100,
        F = 4'b0101, G = 4'b0110, H = 4'b0111, I = 4'b1000;
    always @(w, y_Q)
    begin: state_table
        case (y_Q)
            A:    if (!w) Y_D = B;
                  else Y_D = F;
            B:    if (!w) Y_D = C;
                  else Y_D = F;
            C:    if (!w) Y_D = D;
                  else Y_D = F;
            D:    if (!w) Y_D = E;
                  else Y_D = F;
            E:    if (!w) Y_D = E;
                  else Y_D = F;
            F:    if (!w) Y_D = B;
                  else Y_D = G;
            G:    if (!w) Y_D = B;
                  else Y_D = H;
            H:    if (!w) Y_D = B;
                  else Y_D = I;
            I:    if (!w) Y_D = B;
                  else Y_D = I;
            default: Y_D = 4'bxxxx;
        endcase
    end // state_table
    always @(posedge Clock)
        if (Resetn == 1'b0)    // synchronous clear
            y_Q <= A;
        else
            y_Q <= Y_D;
    assign z = ((y_Q == E) | (y_Q == I)) ? 1'b1 : 1'b0;
    assign LEDR[3:0] = y_Q;
    assign LEDR[9] = z;
    assign LEDR[8:4] = 5'b0;
endmodule

```

RLT View:

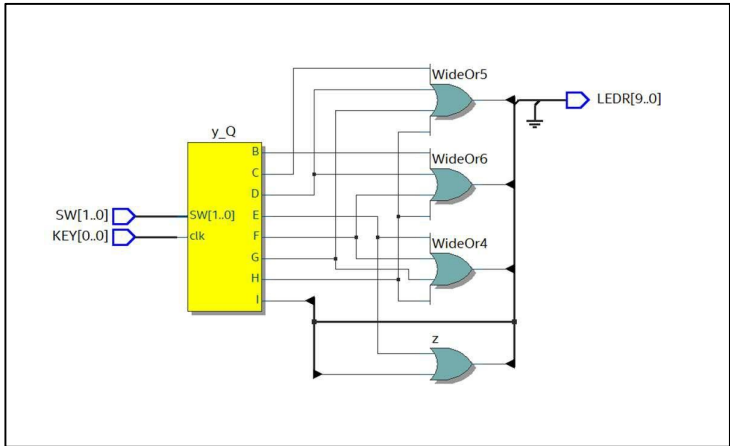

State Machine View:

 

State Transition Tabel:

	Source State	Destination State	Condition
1	A	B	(!SW[1]).(SW[0])
2	A	F	(SW[1]).(SW[0])
3	B	C	(!SW[1]).(SW[0])
4	B	F	(SW[1]).(SW[0])
5	C	D	(!SW[1]).(SW[0])
6	C	F	(SW[1]).(SW[0])
7	D	E	(!SW[1]).(SW[0])
8	D	F	(SW[1]).(SW[0])
9	E	E	(!SW[1]).(SW[0])
10	E	F	(SW[1]).(SW[0])
11	F	B	(!SW[1]).(SW[0])
12	F	G	(SW[1]).(SW[0])
13	G	B	(!SW[1]).(SW[0])
14	G	H	(SW[1]).(SW[0])
15	H	B	(!SW[1]).(SW[0])
16	H	I	(SW[1]).(SW[0])
17	I	B	(!SW[1]).(SW[0])
18	I	I	(SW[1]).(SW[0])

PART 3

Program:

```

module part3 (clk,rst,w,z,sr0,sr1);
    input clk,rst,w;
    output reg z;
    output reg [3:0] sr0,sr1;

    always @(posedge clk or negedge rst) begin
        if (!rst)
            sr0 <= 4'b0000;
        else
            sr0 <= {sr0[2:0], ~w};
        end


    always @(posedge clk or negedge rst) begin
        if (!rst)
            sr1 <= 4'b0000;
        else
            sr1 <= {sr1[2:0], w};
        end

    always @(sr0 or sr1) begin
        z = (sr0 == 4'b0000) || (sr1 == 4'b1111);
    end

endmodule

```

RLT View:

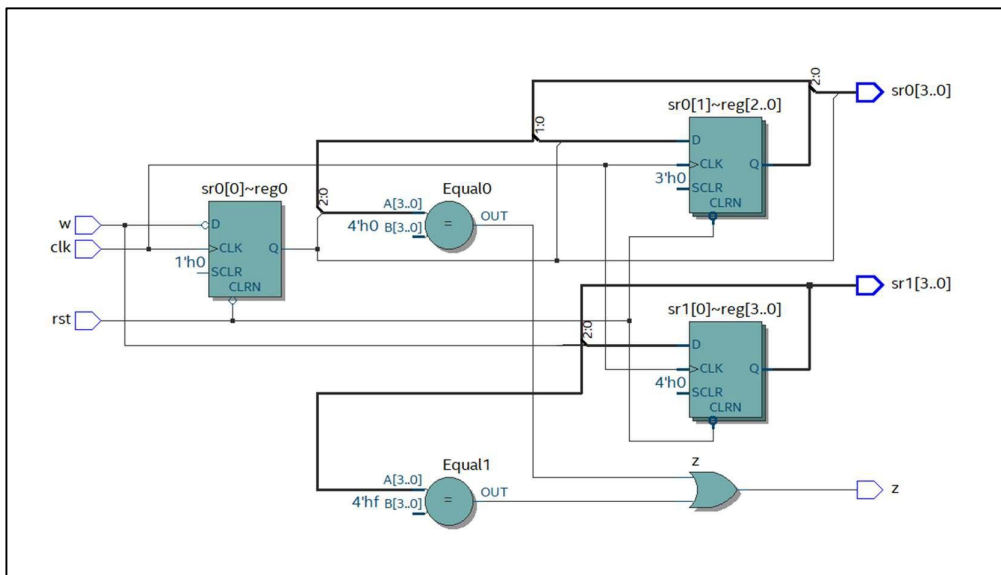

PART 4

Program:

// This is a Morse code encoder circuit. It displays the Morse code for
// letters A to H on LEDR[0]. The letter to be displayed is selected using
// SW[3..0], using A = 000, B = 001, ..., H = 111.

module part4 (SW, CLOCK_50, KEY, LEDR);

/***/

/*** PARAMETER DECLARATIONS ***/

/***/

// SW switch patterns, Morse codes, and code lengths are defined below (in the Morse
 // code, 0 = dot, 1 = dash)

parameter A_SW = 3'b000, A_MORSE = 4'b0010, A_LENGTH = 3'd2; /* .- */

parameter B_SW = 3'b001, B_MORSE = 4'b0001, B_LENGTH = 3'd4; /* -... */

parameter C_SW = 3'b010, C_MORSE = 4'b0101, C_LENGTH = 3'd4; /* -. */

parameter D_SW = 3'b011, D_MORSE = 4'b0001, D_LENGTH = 3'd3; /* -- */

parameter E_SW = 3'b100, E_MORSE = 4'b0000, E_LENGTH = 3'd1; /* . */

parameter F_SW = 3'b101, F_MORSE = 4'b0100, F_LENGTH = 3'd4; /* ... */

parameter G_SW = 3'b110, G_MORSE = 4'b0011, G_LENGTH = 3'd3; /* --. */

parameter H_SW = 3'b111, H_MORSE = 4'b0000, H_LENGTH = 3'd4; /* */

parameter s_WAIT_SEND = 3'b000, s_WAIT_BLANK = 3'b001, s_SEND_DOT = 3'b010,

s_SEND_DASH_1 = 3'b011, s_SEND_DASH_2 = 3'b100,

s_SEND_DASH_3 = 3'b101,

s_RELEASE_SEND = 3'b110;

/***/

/*** PORT DECLARATIONS ***/

/***/

input [2:0] SW;

input [1:0] KEY;

input CLOCK_50;

output [9:0] LEDR;

/***/

/*** LOCAL WIRE DECLARATIONS ***/

/***/

wire Clock, Resetn, go, half_sec_enable, load_regs, shift_and_count, light_on;

reg [3:0] morse_code;

reg [2:0] morse_length;

reg [3:0] send_data;

reg [2:0] data_size;

wire [1:0] pulse_cycle;

reg [3:0] y_Q, Y_D;

/***/

/*** IMPLEMENTATION ***/

```

/*****/
assign Clock = CLOCK_50;
assign Resetn = KEY[0];
assign go = ~KEY[1];

// FSM State Table
always @(go, y_Q, send_data, data_size, half_sec_enable)
begin: state_table
    case (y_Q)
        s_WAIT_SEND:
            if (go) Y_D = s_WAIT_BLANK;
            else Y_D = s_WAIT_SEND;
        s_WAIT_BLANK:// sync with the half-second pulses
            if (!half_sec_enable)
                Y_D = s_WAIT_BLANK;
            else if (send_data[0] == 1'b0)
                Y_D = s_SEND_DOT;
            else
                Y_D = s_SEND_DASH_1;
        s_SEND_DOT:        // wait here for one half-second period
            if (!half_sec_enable)
                Y_D = s_SEND_DOT;
            else if (data_size == 'd1) // check if we are done with this letter
                Y_D = s_RELEASE_SEND;
            else
                Y_D = s_WAIT_BLANK;
        s_SEND_DASH_1:    // wait for three half-second periods
            if (!half_sec_enable)
                Y_D = s_SEND_DASH_1;
            else
                Y_D = s_SEND_DASH_2;
        s_SEND_DASH_2:    // wait for two more half-second periods
            if (!half_sec_enable)
                Y_D = s_SEND_DASH_2;
            else
                Y_D = s_SEND_DASH_3;
        s_SEND_DASH_3:    // wait for one more half-second period
            if (!half_sec_enable)
                Y_D = s_SEND_DASH_3;
            else if (data_size == 'd1) // check if we are done with this letter
                Y_D = s_RELEASE_SEND;
            else
                Y_D = s_WAIT_BLANK;
        s_RELEASE_SEND:
            if (~go) Y_D = s_WAIT_SEND;
            else Y_D = s_RELEASE_SEND;

        default: Y_D = 3'bxxx;
    endcase
end

```

```

        endcase
    end // state_table

    // FSM State flip-flops
    always @(posedge Clock)
        if (Resetn == 1'b0)    // synchronous clear
            y_Q <= s_WAIT_SEND;
        else
            y_Q <= Y_D;

    // FSM outputs
    // turn on the Morse code light in the states below
    assign light_on = (y_Q == s_SEND_DOT) | (y_Q == s_SEND_DASH_1) |
        (y_Q == s_SEND_DASH_2) | (y_Q == s_SEND_DASH_3);
    // specify when to load the Morse code into the shift register, and length into the counter
    assign load_regs = (y_Q == s_WAIT_SEND) & go;
    // specify when to shift the Morse code bits and decrement the length counter
    assign shift_and_count = ((y_Q == s_SEND_DOT) | (y_Q == s_SEND_DASH_3)) &
half_sec_enable;

    /* Create an enable signal that is asserted once every 0.5 of a second. */
    modulo_counter half_sec( .Clock(CLOCK_50), .Resetn(Resetn), .rollover(half_sec_enable) );
    defparam half_sec.n = 25;
    defparam half_sec.k = 25000000;

    /* Letter selection */
    always @(*)
    case (SW)
        A_SW: begin morse_code = A_MORSE; morse_length = A_LENGTH; end
        B_SW: begin morse_code = B_MORSE; morse_length = B_LENGTH; end
        C_SW: begin morse_code = C_MORSE; morse_length = C_LENGTH; end
        D_SW: begin morse_code = D_MORSE; morse_length = D_LENGTH; end
        E_SW: begin morse_code = E_MORSE; morse_length = E_LENGTH; end
        F_SW: begin morse_code = F_MORSE; morse_length = F_LENGTH; end
        G_SW: begin morse_code = G_MORSE; morse_length = G_LENGTH; end
        H_SW: begin morse_code = H_MORSE; morse_length = H_LENGTH; end
    endcase

    /* Store the Morse code to be sent in a shift register, and its length in a counter */
    always@(posedge CLOCK_50)
    begin
        if (~Resetn)
            begin
                send_data <= 'd0;
                data_size <= 'd0;
            end
        else
            if (load_regs)

```

```

        begin
            send_data <= morse_code;
            data_size <= morse_length;
        end
        else if (shift_and_count) // shift and decrement when appropriate
        begin
            send_data[2:0] <= send_data[3:1];
            send_data[3] <= 1'b0;
            data_size <= data_size - 1'b1;
        end
    end

    assign LEDR[0] = light_on;
    assign LEDR[9:1] = 9'b0;
endmodule

module modulo_counter(Clock, Resetn, rollover);
    /**
     * ****
     * PARAMETER DECLARATIONS
     * ****
     */
    parameter          n = 4;
    parameter          k = 16;


    /**
     * ****
     * PORT DECLARATIONS
     * ****
     */
    input  Clock, Resetn;
    output rollover;
    reg    [n-1:0] Q;

    /**
     * ****
     * IMPLEMENTATION
     * ****
     */
    always@(posedge Clock)
    begin
        if (!Resetn)
            Q <= 'd0;
        else if (Q == k-1)
            Q <= 'd0;
        else
            Q <= Q + 1'b1;
    end


    assign rollover = (Q == k-1);
endmodule

```

RLT View:

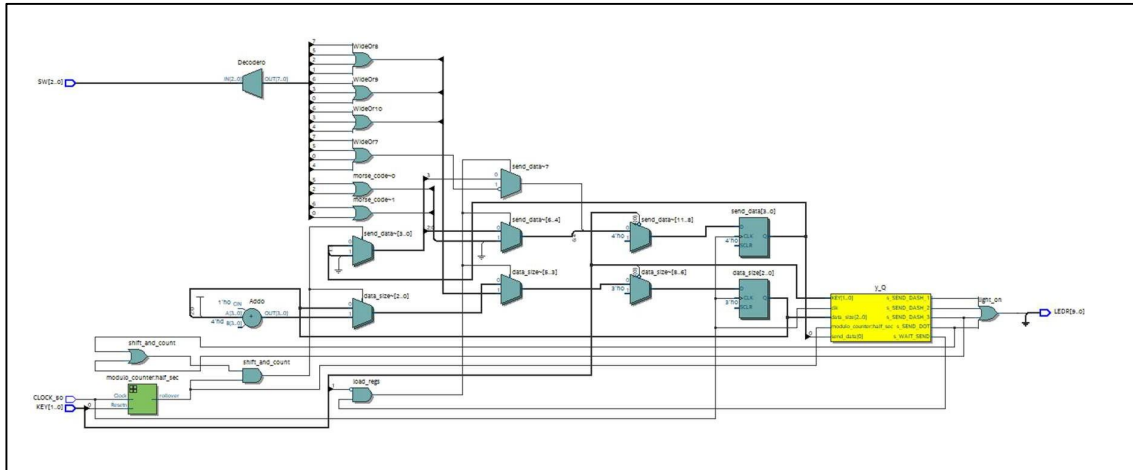

State Transition View:

 

Transition Table:

Source State	Destination State	Condition
1 s_RELEASE_SEND	s_WAIT_SEND	!(KEY[1]) && (KEY[0]) + (KEY[1])
2 s_RELEASE_SEND	s_RELEASE_SEND	!(KEY[1]) && (KEY[0])
3 s_SEND_DASH_1	s_WAIT_SEND	!(KEY[0])
4 s_SEND_DASH_1	s_SEND_DASH_2	(modulo_counter:half_sec).(KEY[0])
5 s_SEND_DASH_1	s_SEND_DASH_1	!(modulo_counter:half_sec).(KEY[0])
6 s_SEND_DASH_2	s_WAIT_SEND	!(KEY[0])
7 s_SEND_DASH_2	s_SEND_DASH_3	(modulo_counter:half_sec).(KEY[0])
8 s_SEND_DASH_2	s_SEND_DASH_2	!(modulo_counter:half_sec).(KEY[0])
9 s_SEND_DASH_3	s_WAIT_SEND	!(KEY[0])
10 s_SEND_DASH_3	s_SEND_DASH_3	!(modulo_counter:half_sec).(KEY[0])
11 s_SEND_DASH_3	s_WAIT_BLANK	!(data_size[0]).(modulo_counter:half_sec).(KEY[0]) + (data_size[0]).(data_size[1]).(data_size[2]).(modulo_counter:half_sec).(KEY[0]) + (data_size[0]).(data_size[1]).(modulo_counter:half_sec).(KEY[0])
12 s_SEND_DASH_3	s_RELEASE_SEND	(data_size[0]).(data_size[1]).(data_size[2]).(modulo_counter:half_sec).(KEY[0])
13 s_SEND_DOT	s_WAIT_SEND	!(KEY[0])
14 s_SEND_DOT	s_WAIT_BLANK	!(data_size[0]).(modulo_counter:half_sec).(KEY[0]) + (data_size[0]).(data_size[1]).(data_size[2]).(modulo_counter:half_sec).(KEY[0]) + (data_size[0]).(data_size[1]).(modulo_counter:half_sec).(KEY[0])
15 s_SEND_DOT	s_RELEASE_SEND	(data_size[0]).(data_size[1]).(data_size[2]).(modulo_counter:half_sec).(KEY[0])
16 s_SEND_DOT	s_SEND_DOT	!(modulo_counter:half_sec).(KEY[0])
17 s_WAIT_BLANK	s_WAIT_SEND	!(KEY[0])
18 s_WAIT_BLANK	s_WAIT_BLANK	!(modulo_counter:half_sec).(KEY[0])
19 s_WAIT_BLANK	s_SEND_DASH_1	(modulo_counter:half_sec).(send_data[0]).(KEY[0])
20 s_WAIT_BLANK	s_SEND_DOT	(modulo_counter:half_sec).(send_data[0]).(KEY[0])
21 s_WAIT_SEND	s_WAIT_SEND	!(KEY[1]) && (KEY[0]) + (KEY[1])
22 s_WAIT_SEND	s_WAIT_BLANK	!(KEY[1]) && (KEY[0])


LABORATORY EXERCISE – 8

PART 1


Program:

```
3 module part1(address,clock,data,wren,q);  
    input clock,wren;  
    input [3:0] data;  
    input [4:0] address;  
    output [3:0] q;  
    Part1 i1(address,clock,data,wren,q);  
Endmodule
```

RLT View:

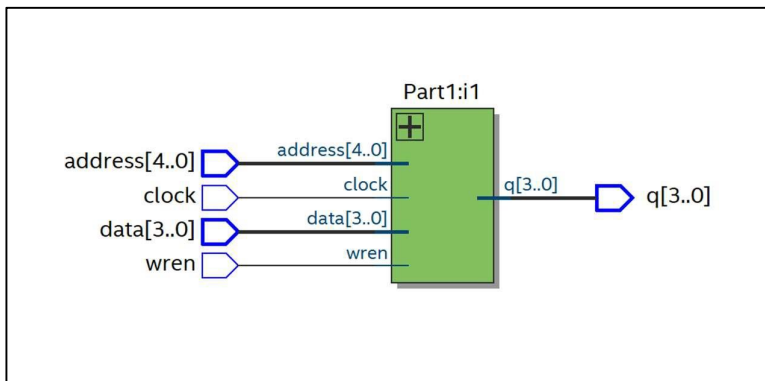

Output Simulation:

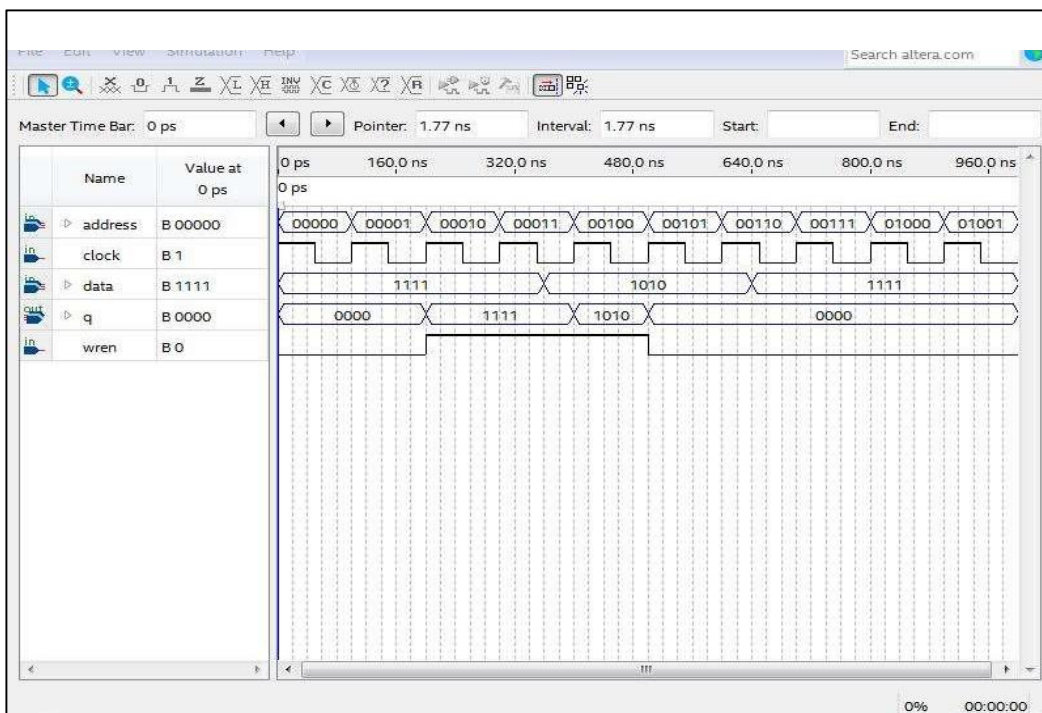

PART 2

Program:

```
// This code instantiates a 32 x 4 memory
//
// inputs: KEY0 is the clock, SW3-SW0 provides data to write into memory.
// SW8-SW4 provides the memory address, SW9 is the memory Write input.
// outputs: 7-seg displays HEX5-4 show the memory address, HEX2
// displays the data input to the memory, and HEX0 show the contents read
// from the memory. LEDGR shows the status of the SW switches.
```

```
module part2 (KEY, SW, HEX5, HEX4, HEX2, HEX0, LEDR);
    input [0:0] KEY;
    input [9:0] SW;
    output [0:6] HEX5, HEX4, HEX2, HEX0;
    output [9:0] LEDR;

    wire Clock, Write;
    wire [4:0] Address;
    wire [3:0] DataIn, DataOut;

    assign Clock = KEY[0];
    assign Write = SW[9];
    assign DataIn = SW[3:0];
    assign Address = SW[8:4];

    // instantiate memory module
    // module ram32x4 (address, clock, data, wren, q);
    ram32x4 U1 (Address, Clock, DataIn, Write, DataOut);

    // display the data input, data output, and address on the 7-segs
    hex7seg digit0 (DataOut[3:0], HEX0);
    hex7seg digit2 (DataIn[3:0], HEX2);
    hex7seg digit5 ({3'b0, Address[4]}, HEX5);
    hex7seg digit4 (Address[3:0], HEX4);

    assign LEDR[3:0] = DataIn;
    assign LEDR[8:4] = Address;
    assign LEDR[9] = Write;
endmodule

//-----
module hex7seg (hex, display);
    input [3:0] hex;
    output [0:6] display;


    reg [0:6] display;
```

```

always @ (hex)
    case (hex)
        4'h0: display = 7'b0000001;
        4'h1: display = 7'b1001111;
        4'h2: display = 7'b0010010;
        4'h3: display = 7'b0000110;
        4'h4: display = 7'b1001100;
        4'h5: display = 7'b0100100;
        4'h6: display = 7'b0100000;
        4'h7: display = 7'b0001111;
        4'h8: display = 7'b0000000;
        4'h9: display = 7'b0000100;
        4'hA: display = 7'b0001000;
        4'hb: display = 7'b1100000;
        4'hC: display = 7'b0110001;
        4'hd: display = 7'b1000010;
        4'hE: display = 7'b0110000;
        4'hF: display = 7'b0111000;
    endcase
endmodule

```

RLT View:

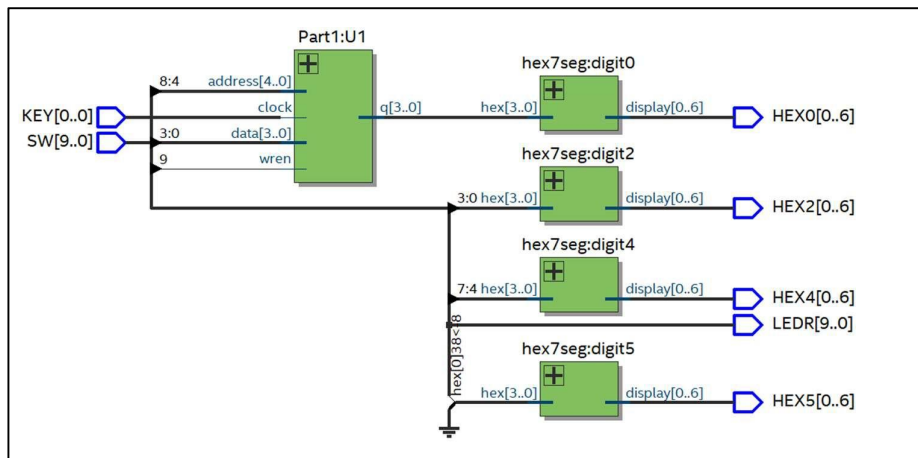

PART 3

Program:

```

//Name: R Yashswini , USN: 1MS21EE043
// This code instantiates a 32 x 4 memory
//
// inputs: KEY0 is the clock, SW3-SW0 provides data to write into memory.
// SW8-SW4 provides the memory address, SW9 is the memory Write input.
// outputs: 7-seg displays HEX5-4 show the memory address, HEX2
// displays the data input to the memory, and HEX0 show the contents read

```

```

// from the memory. LEDR shows the status of the SW switches.
module part3 (KEY, SW, HEX5, HEX4, HEX2, HEX0, LEDR);
    input [0:0] KEY;
    input [9:0] SW;
    output [0:6] HEX5, HEX4, HEX2, HEX0;
    output [9:0] LEDR;

    wire Clock, Write;
    wire [4:0] Address;
    wire [3:0] DataIn, DataOut;

    assign Clock = KEY[0];
    assign Write = SW[9];
    assign DataIn = SW[3:0];
    assign Address = SW[8:4];

    reg [3:0] memory_array [31:0];
    reg [4:0] Address_reg;

    // infer RAM module
    always @(posedge Clock)
    begin
        if (Write)
            memory_array[Address] <= DataIn;
            Address_reg <= Address;
    end
    assign DataOut = memory_array[Address_reg];

    // display the data input, data output, and address on the 7-segs
    hex7seg digit0 (DataOut[3:0], HEX0);
    hex7seg digit1 (DataIn[3:0], HEX2);
    hex7seg digit5 ({3'b0, Address[4]}, HEX5);
    hex7seg digit4 (Address[3:0], HEX4);

    assign LEDR[3:0] = DataIn;
    assign LEDR[8:4] = Address;
    assign LEDR[9] = Write;
endmodule


//-----
module hex7seg (hex, display);
    input [3:0] hex;
    output [0:6] display;

    reg [0:6] display;

    always @ (hex)

```

RLT View:

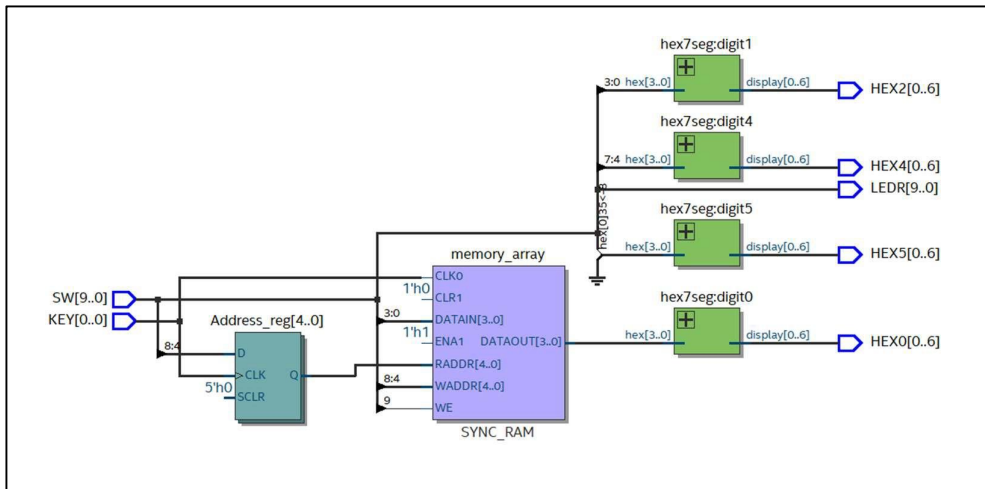

```
// This code implements a simple dual-port memory
//
// inputs: CLOCK_50 is the clock, KEY0 is Resetrn, SW3-SW0 provides data to
// write into memory.
// SW8-SW4 provides the memory address for writing, SW9 is the memory Write input.
```

```

// outputs: 7-seg display HEX5-4 displays the write address, and HEX3-2 shows the read
// address. HEX1 displays the write data and HEX0 shows the read data.
// LEDR shows the status of the SW switches.
module part4 (CLOCK_50, KEY, SW, HEX5, HEX4, HEX3, HEX2, HEX1, HEX0, LEDR);
    input CLOCK_50;
    input [0:0] KEY;
    input [9:0] SW;
    output [0:6] HEX5, HEX4, HEX3, HEX2, HEX1, HEX0;
    output [9:0] LEDR;

    wire Clock, Resetn, Write, Write_sync;
    wire [4:0] Write_address, Write_address_sync;
    wire [3:0] DataIn, DataIn_sync, DataOut;

    assign Resetn = KEY[0];
    assign Clock = CLOCK_50;

    // synchronize all asynchronous inputs to the clock
    regne #(.n(1)) wr_sync_reg(SW[9], Clock, Resetn, 1'b1, Write_sync);
    regne #(.n(1)) wr_reg(Write_sync, Clock, Resetn, 1'b1, Write);
    regne #(.n(5)) addr_sync_reg(SW[8:4], Clock, Resetn, 1'b1, Write_address_sync);
    regne #(.n(5)) addr_reg(Write_address_sync, Clock, Resetn, 1'b1, Write_address);
    regne #(.n(4)) din_sync_reg(SW[3:0], Clock, Resetn, 1'b1, DataIn_sync);
    regne #(.n(4)) din_reg(DataIn_sync, Clock, Resetn, 1'b1, DataIn);

    // one second cycle counter
    parameter m = 25;
    reg [m-1:0] slow_count;
    reg [4:0] Read_address; // cycles from addresses 0 to 31 at one second per address

    // Create a 1Hz 5-bit address counter
    // A large counter to produce a 1 second (approx) enable
    always @(posedge Clock)
        slow_count <= slow_count + 1'b1;
    // the read address counter
    always @ (posedge Clock)
        if (Resetn == 0)
            Read_address <= 5'b0;
        else if (slow_count == 0)
            Read_address <= Read_address + 1'b1;

    // instantiate memory module
    // module ram32x4 (clock, data, rdaddress, wraddress, wren, q);
    ram32x4 U1 (Clock, DataIn, Read_address, Write_address, Write, DataOut);

    // display the data input, data output, and addresses on the 7-segs
    hex7seg digit5 ({3'b0, Write_address[4]}, HEX5);
    hex7seg digit4 (Write_address[3:0], HEX4);

```

```

    hex7seg digit3 ({3'b0, Read_address[4]}, HEX3);
    hex7seg digit2 (Read_address[3:0], HEX2);
    hex7seg digit1 (DataIn[3:0], HEX1);
    hex7seg digit0 (DataOut[3:0], HEX0);

    assign LEDR[3:0] = DataIn;
    assign LEDR[8:4] = Write_address;
    assign LEDR[9] = Write;
endmodule

```

```

module regne (R, Clock, Resetn, E, Q);
    parameter n = 7;
    input [n-1:0] R;
    input Clock, Resetn, E;
    output [n-1:0] Q;
    reg [n-1:0] Q;

```

```

    always @(posedge Clock)
        if (Resetn == 0)
            Q <= {n{1'b0}};
        else if (E)
            Q <= R;

```

```

endmodule

```

```

//-----

```

```

module hex7seg (hex, display);
    input [3:0] hex;
    output [0:6] display;

```

```

    reg [0:6] display;


```

```

    always @ (hex)
        case (hex)
            4'h0: display = 7'b0000001;
            4'h1: display = 7'b1001111;
            4'h2: display = 7'b0010010;
            4'h3: display = 7'b0000110;
            4'h4: display = 7'b1001100;
            4'h5: display = 7'b0100100;
            4'h6: display = 7'b0100000;
            4'h7: display = 7'b0001111;
            4'h8: display = 7'b0000000;
            4'h9: display = 7'b0000100;
            4'hA: display = 7'b0001000;
            4'hb: display = 7'b1100000;
            4'hC: display = 7'b0110001;
            4'hd: display = 7'b1000010;

```

RLT View:

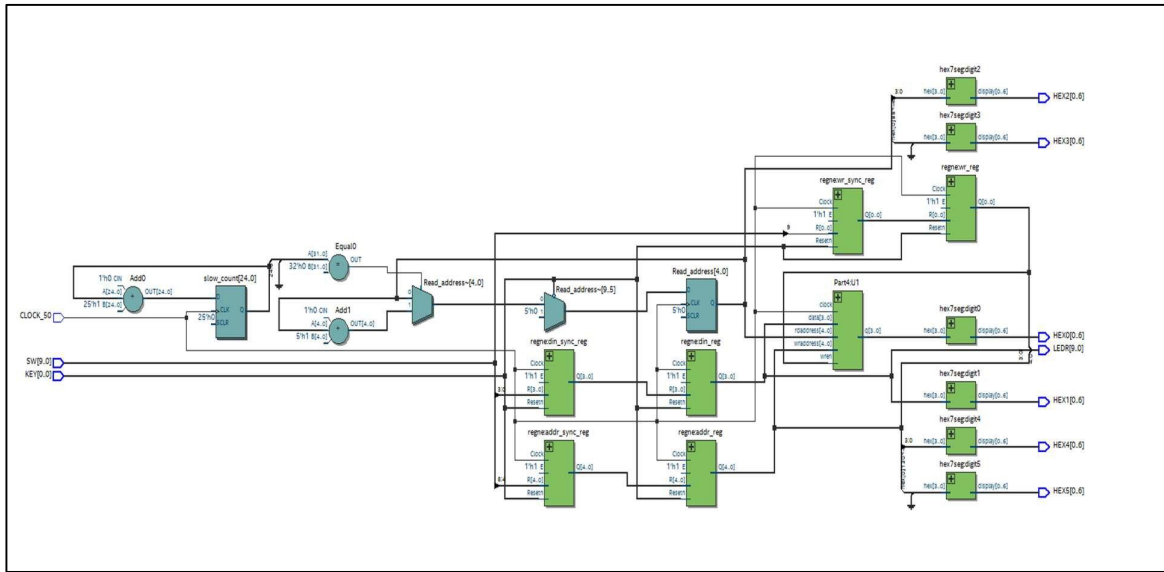

EXP-6

Part-3

// Implements an unsigned multiplier $P = A \times B$.

// inputs: SW11-8 = A, SW3-0 = B

// outputs: HEX5-4 shows the product P, HEX2 shows A, HEX0 shows B

module part3 (SW, HEX5, HEX4, HEX2, HEX0);

input [7:0] SW;

output [0:6] HEX5, HEX4, HEX2, HEX0;

wire [3:0] A, B;

wire [7:0] P;

wire [3:1] C_b1; // carries for row that ANDs with B1

wire [5:2] PP1; // partial products from row that ANDs with B1

wire [3:1] C_b2; // carries for row that ANDs with B2

wire [6:3] PP2; // partial products from row that ANDs with B2

wire [3:1] C_b3; // carries for row that ANDs with B3

assign A = SW[7:4];

assign B = SW[3:0];

assign P[0] = A[0] & B[0];

// module fa (a, b, ci, s, co);

fa b1_a0 (A[1] & B[0], A[0] & B[1], 1'b0, P[1], C_b1[1]);

fa b1_a1 (A[2] & B[0], A[1] & B[1], C_b1[1], PP1[2], C_b1[2]);

fa b1_a2 (A[3] & B[0], A[2] & B[1], C_b1[2], PP1[3], C_b1[3]);

fa b1_a3 (1'b0, A[3] & B[1], C_b1[3], PP1[4], PP1[5]);

// module fa (a, b, ci, s, co);

fa b2_a0 (PP1[2], A[0] & B[2], 1'b0, P[2], C_b2[1]);

fa b2_a1 (PP1[3], A[1] & B[2], C_b2[1], PP2[3], C_b2[2]);

fa b2_a2 (PP1[4], A[2] & B[2], C_b2[2], PP2[4], C_b2[3]);

fa b2_a3 (PP1[5], A[3] & B[2], C_b2[3], PP2[5], PP2[6]);

// module fa (a, b, ci, s, co);

fa b3_a0 (PP2[3], A[0] & B[3], 1'b0, P[3], C_b3[1]);

fa b3_a1 (PP2[4], A[1] & B[3], C_b3[1], P[4], C_b3[2]);

fa b3_a2 (PP2[5], A[2] & B[3], C_b3[2], P[5], C_b3[3]);

fa b3_a3 (PP2[6], A[3] & B[3], C_b3[3], P[6], P[7]);

// drive the displays through a 7-seg decoders

hex7seg digit_5 (P[7:4], HEX5);

hex7seg digit_4 (P[3:0], HEX4);

hex7seg digit_3 (A, HEX2);

hex7seg digit_2 (B, HEX0);

endmodule

module fa (a, b, ci, s, co);

input a, b, ci;

output s, co;

wire a_xor_b;

assign a_xor_b = a ^ b;

assign s = a_xor_b ^ ci;

assign co = (~a_xor_b & b) | (a_xor_b & ci);

endmodule

module hex7seg (hex, display);

input [3:0] hex;

```

output [0:6] display;

reg [0:6] display;

always @(hex)
    case (hex)
        4'h0: display = 7'b0000001;
        4'h1: display = 7'b1001111;
        4'h2: display = 7'b0010010;
        4'h3: display = 7'b0000110;
        4'h4: display = 7'b1001100;
        4'h5: display = 7'b0100100;
        4'h6: display = 7'b0100000;
        4'h7: display = 7'b0001111;
        4'h8: display = 7'b0000000;
        4'h9: display = 7'b0000100;
        4'hA: display = 7'b0001000;
        4'hb: display = 7'b1100000;
        4'hC: display = 7'b0110001;
        4'hd: display = 7'b1000010;
        4'hE: display = 7'b0110000;
        4'hF: display = 7'b0111000;
    endcase
endmodule

```

PART-4

```

// Implements an unsigned multiplier P = A x B.
// inputs: SW7-0, SW9 select A, SW8 selects B, KEY[0] is reset, KEY[1] is clock
// outputs:      HEX3-0 shows the product P
module part4 (SW, KEY, LEDR, HEX3, HEX2, HEX1, HEX0);
    input [9:0] SW;
    input [1:0] KEY;
    output [9:0] LEDR;
    output [0:6] HEX3, HEX2, HEX1, HEX0;

    wire Resetn, Clock;
    reg [7:0] A, B;
    reg [15:0] P_reg;
    wire [15:0] PP0, PP1, PP2, PP3, PP4, PP5, PP6;
    wire [15:0] P;

    assign Resetn = KEY[0];
    assign Clock = KEY[1];
    always @(posedge Clock)
    begin
        if (~Resetn)
            begin
                A <= 8'b0; B <= 8'b0; P_reg <= 16'b0;
            end
        else
            begin
                if (SW[9])      A <= SW[7:0];
                if (SW[8])      B <= SW[7:0];
                P_reg <= P;
            end
        end
    end

    assign LEDR[7:0] = SW[9] ? A : (SW[8] ? B : 8'b0);
    assign LEDR[9:8] = SW[9:8];

    assign PP0 = { 8'd0, A & {8{B[0]}} };
    assign PP1 = PP0 + { 7'd0, A & {8{B[1]}} , 1'd0 };

```

```

assign PP2 = PP1 + { 6'd0, A & {8{B[2]}}, 2'd0 };
assign PP3 = PP2 + { 5'd0, A & {8{B[3]}}, 3'd0 };
assign PP4 = PP3 + { 4'd0, A & {8{B[4]}}, 4'd0 };
assign PP5 = PP4 + { 3'd0, A & {8{B[5]}}, 5'd0 };
assign PP6 = PP5 + { 2'd0, A & {8{B[6]}}, 6'd0 };
assign P = PP6 + { 1'd0, A & {8{B[7]}}, 7'd0 };

// drive the display through a 7-seg decoder
hex7seg digit_3 (P_reg[15:12], HEX3);
hex7seg digit_2 (P_reg[11:8], HEX2);
hex7seg digit_1 (P_reg[7:4], HEX1);
hex7seg digit_0 (P_reg[3:0], HEX0);
endmodule

```

```

module hex7seg (hex, display);
    input [3:0] hex;
    output [0:6] display;

    reg [0:6] display;

    always @(hex)
        case (hex)
            4'h0: display = 7'b0000001;
            4'h1: display = 7'b1001111;
            4'h2: display = 7'b0010010;
            4'h3: display = 7'b0000110;
            4'h4: display = 7'b1001100;
            4'h5: display = 7'b0100100;
            4'h6: display = 7'b0100000;
            4'h7: display = 7'b0001111;
            4'h8: display = 7'b0000000;
            4'h9: display = 7'b0001100;
            4'hA: display = 7'b0001000;
            4'hb: display = 7'b1100000;
            4'hC: display = 7'b0110001;
            4'hd: display = 7'b1000010;
            4'hE: display = 7'b0110000;
            4'hF: display = 7'b0111000;
        endcase
endmodule

```

PART-5

```

// Implements an unsigned multiplier P = A x B.
// inputs: SW7-0, SW9 select A, SW8 selects B, KEY[0] is reset, KEY[1] is clock
// outputs:      HEX3-0 shows the product P
module part5 (SW, KEY, LEDR, HEX3, HEX2, HEX1, HEX0);
    input [9:0] SW;
    input [1:0] KEY;
    output [9:0] LEDR;
    output [0:6] HEX3, HEX2, HEX1, HEX0;

    wire Resetn, Clock;
    reg [7:0] A, B;
    reg [15:0] P_reg;
    wire [15:0] PP0, PP1, PP2, PP3, PP4, PP5, PP6;
    wire [15:0] P;

    assign Resetn = KEY[0];
    assign Clock = KEY[1];
    always @(posedge Clock)
        begin
            if (~Resetn)
                begin

```

```

        A <= 8'b0; B <= 8'b0; P_reg <= 16'b0;
    end
    else
    begin
        if (SW[9])      A <= SW[7:0];
        if (SW[8])      B <= SW[7:0];
        P_reg <= P;
    end
end

assign LEDR[7:0] = SW[9] ? A : (SW[8] ? B : 8'b0);
assign LEDR[9:8] = SW[9:8];

assign PP0 = { 8'd0, A & {8{B[0]}} } + { 7'd0, A & {8{B[1]}} , 1'd0 };
assign PP1 = { 6'd0, A & {8{B[2]}} , 2'd0 } + { 5'd0, A & {8{B[3]}} , 3'd0 };
assign PP2 = { 4'd0, A & {8{B[4]}} , 4'd0 } + { 3'd0, A & {8{B[5]}} , 5'd0 };
assign PP3 = { 2'd0, A & {8{B[6]}} , 6'd0 } + { 1'd0, A & {8{B[7]}} , 7'd0 };
assign PP4 = PP0 + PP1;
assign PP5 = PP2 + PP3;
assign P = PP4 + PP5;

// drive the displays through 7-seg decoders
hex7seg digit_3 (P_reg[15:12], HEX3);
hex7seg digit_2 (P_reg[11:8], HEX2);
hex7seg digit_1 (P_reg[7:4], HEX1);
hex7seg digit_0 (P_reg[3:0], HEX0);
endmodule

module hex7seg (hex, display);
    input [3:0] hex;
    output [0:6] display;

    reg [0:6] display;

    always @ (hex)
        case (hex)
            4'h0: display = 7'b0000001;
            4'h1: display = 7'b1001111;
            4'h2: display = 7'b0010010;
            4'h3: display = 7'b0000110;
            4'h4: display = 7'b1001100;
            4'h5: display = 7'b0100100;
            4'h6: display = 7'b0100000;
            4'h7: display = 7'b0001111;
            4'h8: display = 7'b0000000;
            4'h9: display = 7'b0001100;
            4'hA: display = 7'b0001000;
            4'hb: display = 7'b1100000;
            4'hC: display = 7'b0110001;
            4'hd: display = 7'b1000010;
            4'hE: display = 7'b0110000;
            4'hF: display = 7'b0111000;
        endcase
endmodule

```